



Advanced
Micro
Devices

A High
Performance
Disc
Controller

\$5.00

DATA, ADDRESS, CONTROL BUS

REGISTERS

BUS
INTERFACE

M BUS


CONTROL
STORE

BIT
SLICES

DISC
INTERFACE

SEQUENCER

DISC
DRIVE

 

A HIGH PERFORMANCE DISC CONTROLLER

INTRODUCTION

The Am2901A Four-Bit Bipolar Microprocessor Slice, a significant advance in the state-of-the-art technology in Low-Power Schottky Integrated Circuits, enables the Design Engineer to implement new systems with higher logic density, better cost-effectiveness, and improved product versatility. The higher logic density and better cost-effectiveness of microprocessor-based designs is well-known and will not be discussed here. This application note, describing a Pertec D3441 Disc Controller for the Digital Equipment Corporation (DEC) PDP-11, will demonstrate how improved product versatility can be achieved by employing the Am2901A in the design of a peripheral controller.

This disc controller design is not intended to be an example of a minimal logic, cost-effective controller only one step away from the marketplace. Instead, think of it as the grandfather. Its large, writeable microprogram control store and its generalized disc and UNIBUS interface make it suitable to be the prototype for a family of disc controllers. Individual controllers would use ROM's of the appropriate size for the control store, and the disc interface would be tailored to a particular disc drive.

THE DISC CONTROLLER

A major advantage of designing with microprocessors is that the designs tend to be highly structured and therefore much easier to comprehend. Referring to Figure 1, notice that the disc controller is composed of a small number of well-defined sub-sections. Each sub-section will be discussed in detail and then the interaction between sub-sections will be described. The reader will find that the individual sub-sections are easy to understand because each one has a limited but well-defined role in the disc controller.

THE MICROPROCESSOR

The microprocessor, 8 bits wide using two Am2901A's, provides the disc controller with an arithmetic and logic capability. In this application, the arithmetic capabilities of the Am2901A are not taxed. Mainly, they are used to generate checksums on disc reads. The principal role of the microprocessor in this design is that of a logic processor. As the reader will discover further on, both the DEC UNIBUS interface and the disc interface are very general purpose. It is the logic processing power of the Am2901A, coupled with the control information of the microprogram, that enables the disc controller to completely emulate the RK11 disc controller (SSI TTL controller from DEC). If the disc controller is considered as a state machine, at any given instance, the current state of the machine is to a large degree defined by the contents of the microprogram register. When an unexpected state is encountered, the logic processing power of the microprocessor enables it to exercise more control over the selection of the next state to enter. In the disc controller, this is evidenced more through error recovery procedures.


All recoverable errors can be handled by the disc controller without the intervention of the host computer. In addition to supplying logic processing power, the microprocessor also provides seventeen high-speed, 8-bit temporary storage registers. Most of these registers are assigned specific functions. In this application, twelve registers were used to build six 16-bit registers. These registers contain the disc address, memory address, transfer word count, control and status information, error information, and the checksum. Of the remaining five registers, four are utility registers that are employed as needed, and the fifth is the Q register which can be used to store and retrieve 8-bit values.

Figure 2, depicting the two Am2901A's, shows that the microprocessor interface to the other sub-sections is very simple. The 8-bit bidirectional M bus (microprocessor bus) enables the microprocessor to input/output data from/to the other subsections of the disc controller. Four condition lines (ZERO, MINUS, OVRFL, and CARRY) communicate the results of logic and arithmetic operations to the sequencer, which may select one of these lines to determine the address of the next microinstruction. Notice that since the condition lines are latched, the sequencer is always looking at the conditions of the previous microinstruction. On each clock cycle, the Am2901A's are presented with a 19-bit instruction from the microprogram register. This 19-bit instruction consists of a 9-bit microinstruction decode, an 8-bit register select, the carry-in, and the output enable (see Figure 3). By the end of the clock cycle, the specified arithmetic or logic operation has been performed, the result has been stored, and the condition codes have been latched. The microprocessor is now ready to perform the next instruction.

THE SEQUENCER

A microinstruction usually has two primary parts. These are: (1) the definition and control of all elemental micro-operations to be performed, and (2) the definition of the address of the next microinstruction to be executed. Referring back to the consideration of the disc controller as a state machine, it is evident that the controller's ability to perform any useful function is dependent on its ability to progress from state to state in a controller manner. It is the task of the sequencer to provide control over the transitions from state to state.

In order to provide this control, some feedback from various system components is necessary. For example, when reading a word from PDP-11 main memory, the controller must first request the UNIBUS by asserting NPR (non-processor request). The controller then enters a waiting state and the sequencer will keep the controller in this state until the signal NPR RDY informs the sequencer that the UNIBUS is now available for the transfer. At this time, the sequencer will transition the controller into the next state which would start driving the address onto the UNIBUS and assert MSYN (master sync). The sequencer designed for this controller (see Figure 2) provides for up to sixteen different input condi-

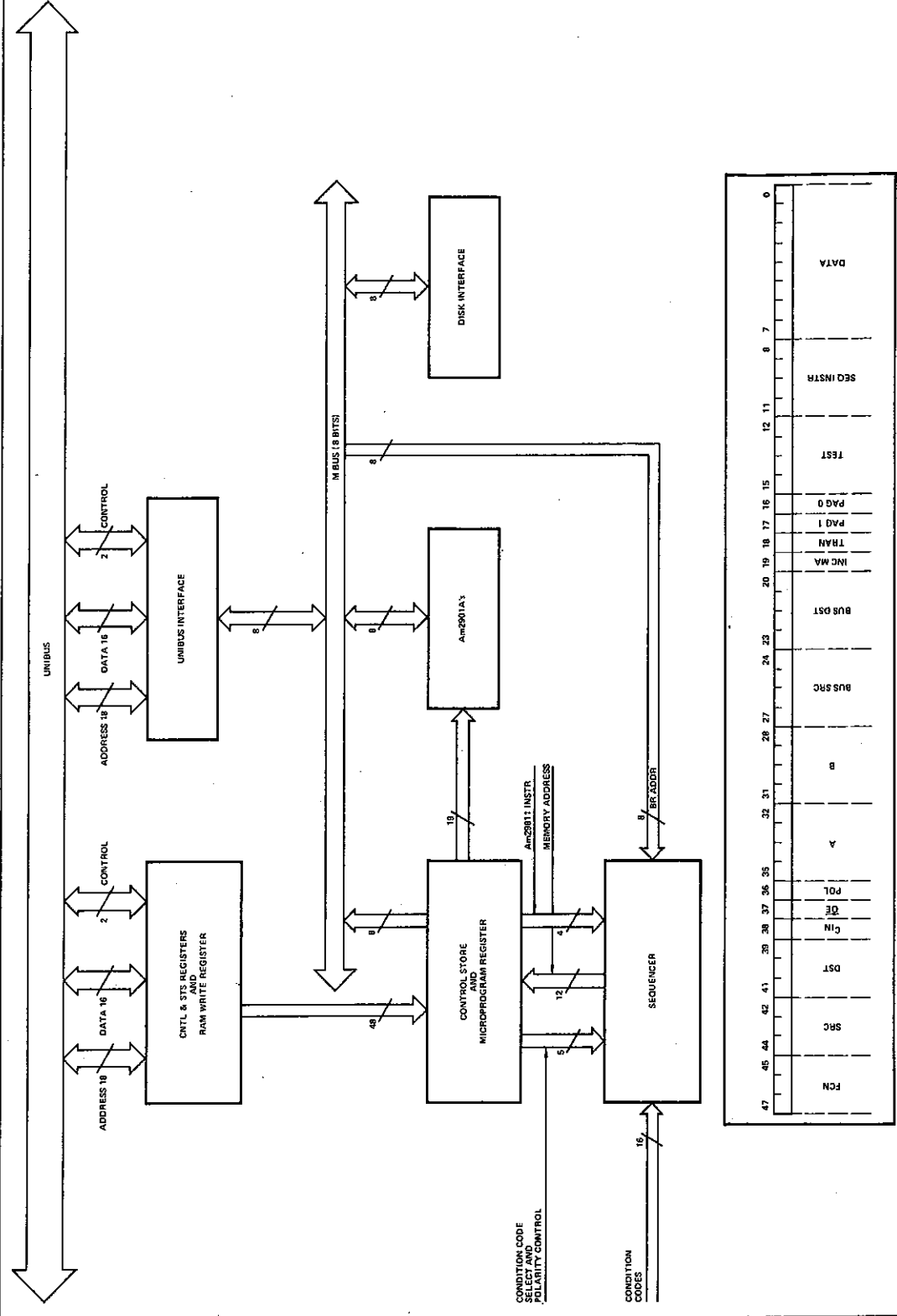

MICROCODE BIT ASSIGNMENTS

Figure 1.

18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
DESTINATION CONTROL			ALU FUNCTION			ALU SOURCE			A REGISTER ADDRESS				B REGISTER ADDRESS				C A R R Y	O U N T A B L E
MICROINSTRUCTION DECODE									REGISTER SELECT									

Figure 3.

tions. On each microcycle, four bits from the microprogram register will select one of the sixteen input conditions. The selected condition is XOR'ed with another bit from the microprogram register to provide polarity control over the selected conditions as it is inputted to the Am29811.

The Am29811, the next address control unit, can execute sixteen different next address control functions, most of which are conditional. Thus, the device requires four instruction inputs as well as the condition code test input. The four instruction inputs come from a multiplexer that normally selects the Am29811 instruction specified in the microprogram register. However, when the writeable control store is being loaded, the multiplexer selects the other input, which forces the Am29811 to execute JUMP ZERO on the first write cycle and CONTINUE on all following write cycles.

The outputs of the Am29811 are used to control the stack pointer and the next address multiplexer of the three Am2911's. These three Am2911's are cascaded to form the 12-bit microprogram sequencer. The Am2911's can select an address from any of three sources. They are: (1) external data from the D inputs, stored in an internal register; (2) a four-word deep push/pop stack; or (3) a program counter register (which usually contains the last address plus one). The push/pop stack includes certain control lines so that it can efficiently execute nested subroutine linkages. The internal register that is loaded from the M bus appears to the rest of the system as just another M bus destination. At the end of a bus cycle, if the two low-order Am2911's or the high-order Am2911 has been selected as the M bus destination, the selected Am2911's register enable will be strobed to clock in the data on the M bus. Once the internal register is loaded, it can be selected on any following microinstruction as the source of the next address.

THE CONTROL STORE

The output of the microprogram sequencer is a 12-bit address that selects the next microinstruction to be fetched from the control store. At the beginning of each microcycle, the output of the control store is strobed into the microprogram register. Since this register holds the microinstruction while it is being executed, the memory is free to fetch the next microinstruction as soon as the sequencer can determine the address of the next instruction. This technique, referred to as pipelining, allows the fetching of the next microinstruction to be overlapped with the execution of the current microinstruction.

The disc controller's control store, 48 bits wide by 1K deep, is comprised of twelve Am9130's (see Figure 4). The Am9130 is a high-performance, low-power, 4096-bit, static, read/write memory organized as 1024 words by 4 bits per word. The data input and output signals are bussed together and share common I/O pins.

The microprogram register is comprised of six 8-bit registers. The low-order register holds the data portion of each microinstruction. This register, an Am25LS374, has three-state outputs and when selected as a bus source, it will drive the data onto the M bus. The other five registers are Am25LS273's, which consist of D-type flip-flops with a common clock and a common clear.

Normally, the control store is clocked by the microprocessor clock (μ PCLK). However, when the control store is being loaded by the PDP-11, it is clocked every time a 48-bit word, assembled in the RAM Write Register, is ready to be written into the control store. When a millisecond has passed without a RAM write cycle, a one-shot times out (the signal LD MCODE is no longer asserted), and the control store is once again clocked by μ PCLK. While LD MCODE was asserted, the clear input to the microprogram register was also asserted and the output of the Am9130's was disabled.

THE CONTROL AND STATUS REGISTERS

To provide for communication between the PDP-11 CPU and the disc controller, sixteen 16-bit registers have been interfaced to the UNIBUS (see Figure 5). Except for the fact that the last two registers play a special role in loading the control store (determining the address of these registers on the UNIBUS) and in selecting the frequency of the μ PCLK, these registers are just memory locations. Indeed, core memory locations could be used for the control and status registers. The only disadvantage to doing this would be that the controller would not be compatible with existing software.

The disc controller uses the same procedure for reading or writing the control and status registers as it does when reading or writing in main memory. This approach has the advantage of using the UNIBUS arbitration logic to solve the problem of both the CPU and the controller accessing the same control and status register at the same time.

Since the control and status registers are just memory locations, the definition of what each group of bits means is totally determined by the microprogram. As the same controller is used to interface different types of disc drives, the microcode can define the control and status registers to be compatible with whatever PDP-11 disc system is to be emulated.

As was mentioned earlier, the last two registers are special. When data is written into the last register, it is also stored in one of the RAM WRITE REGISTERS. Which register is selected is determined by a 2-bit counter that is incremented after each write. Every fourth write is a signal that 48 bits have been accumulated in the RAM WRITE REGISTER and it is time for the control store to perform a write cycle. Example 1 is a listing of PDP-11 code that would load the control store from a 3K word buffer in main memory.

```

;LOADCS is entered with R0 a pointer to the buffer
;and R1 a pointer to the last device register (160016).
LOADCS:  RESET                ;initialize 2-bit counter and
                                ;cause LDMCODE to be asserted
LOOP:    MOV (R0)+, (R1)       ;load 48-bit RAM
         MOV (R0)+, (R1)       ;WRITE REGISTER
         MOV (R0)+, (R1)
         CLR (R1)              ;phony write to cause control store write
         CMP R0, #BUFEND      ;condition : has all of the buffer been copied?
         BLO LOOP             ;if no, then branch
         RTS PC                ;if yes, then return

```

Example 1. PDP-11 Code to Load Control Store.

Whenever the second to last register is written, the data is also stored in a 16-bit internal register. The high-order byte is used to set the UNIBUS address of the control and status registers. Initially, the base device register address was 160000₈, because the INIT pulse on the UNIBUS (caused by power-up or the RESET instruction) cleared the 16-bit internal register. It is up to the PDP-11 to keep track of the current address of the control and status registers as they are moved about. Also, the PDP-11 must somehow let the controller know where its registers are. Usually, this information is contained in the microcode. This ability to change the address of the device registers allows the controller to attempt to emulate just about whatever it wants to emulate.

The low-order four bits of this internal register can be set by the PDP-11 to select 1-of-16 microprocessor clock rates. It is not clear that this is very useful, but in a general purpose prototyping design, why not?

THE UNIBUS INTERFACE

The UNIBUS interface consists of two main parts: (1) the transceivers for the address, data, and control lines; and (2) the handshaking logic required to control UNIBUS transactions.²

Figure 6, depicting the address, data, and control line transceivers, illustrates that the microprocessor communicates with the transceivers via registers which can act as either sources or destinations for the M bus. The registers for the address line transceivers (in this case used only as line drivers) are synchronous 4-bit counters (Am25LS161). In a DMA transfer, the starting address would be initially loaded into the Am25LS161's in two M bus cycles. On the first cycle, the low-order byte of the address register would be loaded. The second cycle would load the high byte. Once the memory address register has been initialized to the transfer starting address, it can be incremented to successive memory locations at the end of each transfer by the assertion of INC MA. The output of the address register is shifted one bit position as it is fed into the UNIBUS drivers to compensate for the fact that each byte has a unique address in the PDP-11, and the controller only addresses word locations.

Am2907's are used as the transceivers for the UNIBUS data lines. Internal to the Am2907's are the data input and the data output registers. On a UNIBUS read cycle, data is strobed into the data input register from the UNIBUS when S_{SYN} (Slave Sync) is received. The data is then available to the

microprocessor via the M bus. On a UNIBUS write cycle, data is first loaded into the data output register via the M bus, and then the UNIBUS write transaction is initiated.

Another Am2907 is used for the control lines and the two high-order address lines. These control and address lines are initialized before the start of a DMA transfer. The control lines never need to be changed during a DMA burst. However, if the memory address register should overflow, the two high-order address bits will need to be updated before the next UNIBUS read or write transaction.

In addition to the address, data, and control lines, the UNIBUS has additional signals which provide synchronization for data transfers, allow control of the UNIBUS to be passed to any DMA controller, and provide an interrupt capability.

Figure 7 is the diagram of the UNIBUS handshaking logic. The microprocessor may request the UNIBUS by asserting NPR REQ or BR REQ, depending on whether the bus is being requested for a DMA transfer or an interrupt transaction. When the handshaking logic has gained control of the UNIBUS, the microprocessor will be informed by the assertion of either NPR RDY or BR RDY. For a read or write transaction, TRAN is asserted to initiate the data transfer. Coming to the microprocessor's aid once again, the handshaking logic will sequence through UNIBUS protocols and inform the microprocessor of the completion of the transfer by asserting TRANSFER DONE.

THE DISC INTERFACE

The disc interface is comprised of a 24-bit parallel input port and a 24-bit parallel output port (Figure 6), and an 8-bit wide, 16-word deep FIFO (Figure 2). The input and output ports are "soft", in that the function of the individual bits are defined in the microcode. Since both ports are quite wide, almost any disc based on 2314 technology can be accommodated by the controller.

The input port receives status information and control signals from the disc drive. Status information generally includes the sector counter, the index and sector pulses, error conditions, and unit attention. Any control signals from the drive that are used to strobe data into registers should be received on a line with a wire-wrap pin. This allows for simple gating of the control signals to generate data strobes.

The output port transmits control information, such as cylinder address, head select, read and write enable, and unit select, to the disc drives.

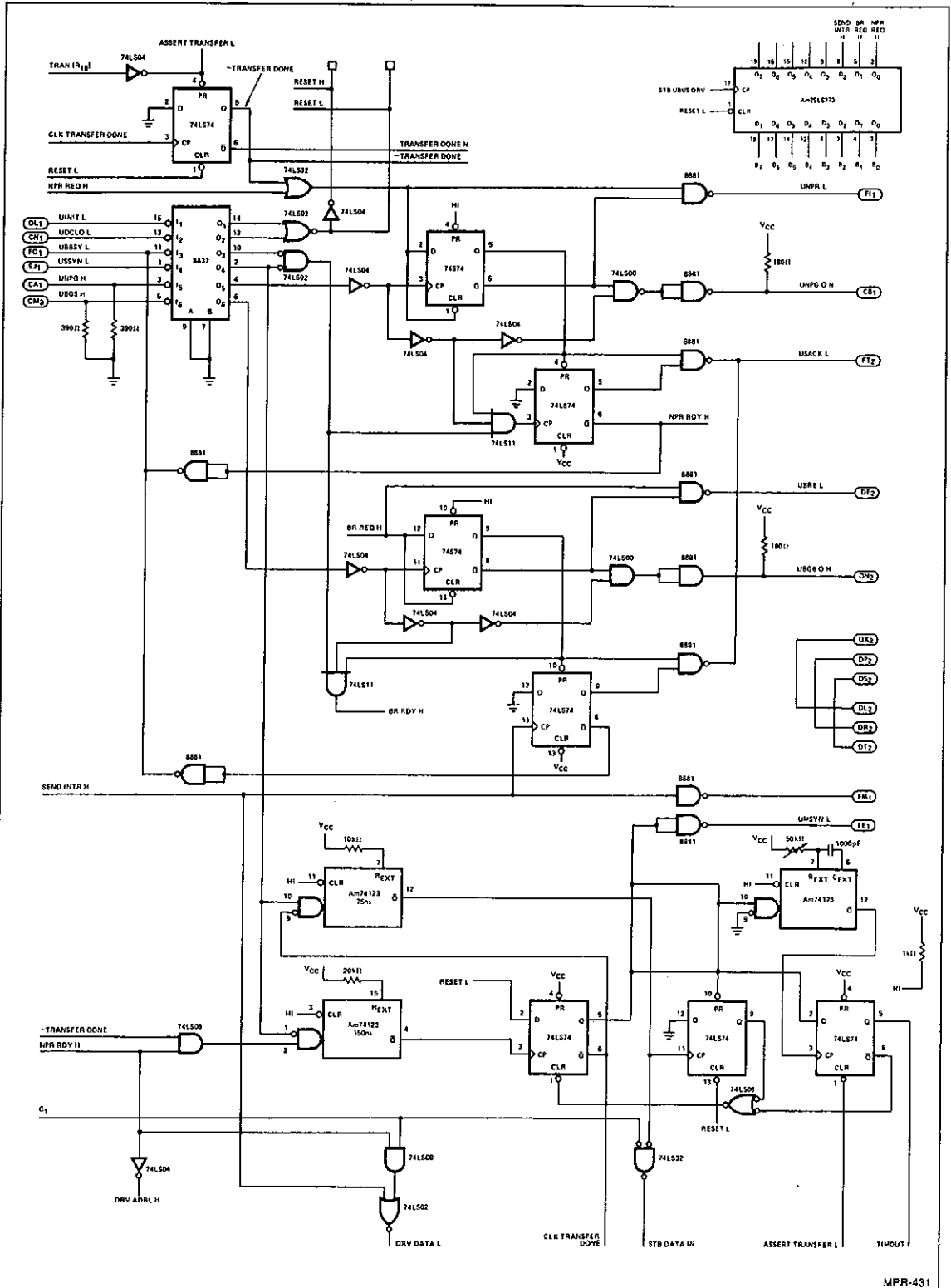


Figure 7.

The FIFO performs parallel-to-serial conversion on data that is being written on the disc and serial-to-parallel conversion on data that is read from the disc. When writing, the FIFO is clocked by a crystal oscillator at whatever frequency is required by the disc drive. However, when reading data from the disc, the FIFO is clocked by the RD CLK signal from the disc drive.

In addition to converting from parallel-to-serial and vice versa, the FIFO provides buffering between the controller and the disc drive. For example, before a disc write is initiated, the 16-word deep FIFO will have been filled. Each time a byte is dispatched to the disc, the contents of the FIFO will shuffle down and the microprocessor will be signalled that there is room for another byte in the FIFO. If the controller experiences a delay in gaining control of the UNIBUS to fetch the next word, the 16-byte buffer within the FIFO will enable it to keep sending serial data to the disc in sync with the write clock. Once the controller gains control of the UNIBUS, it should not release it until enough data has been read from main memory to refill the FIFO.

THE M BUS

The microprocessor bus is the main communication path that links the various subsections of the disc controller together. On each microcycle, the M bus can perform one 8-bit data transfer between a bus source and a bus destination. At the beginning of the microcycle, the selected bus source begins driving data onto the M bus. After a short propagation delay, the data is available to all destinations on the M bus. At the very end of the microcycle, the data on the M bus will be strobed into the selected destinations.

The M bus sources and destinations are selected by 4-bit fields in each microinstruction (refer to Figure 8). Therefore, the M bus can have up to 15 sources and 15 destinations. In addition, the microprocessor can be either a source or a destination. Notice that if the microprocessor is not using the M bus during a microcycle, the M bus is free to perform a data transfer in parallel with whatever the microprocessor is doing. Also, it is sometimes useful for the microprocessor to be a second M bus destination. For example, when the controller is reading data from the disc, as each byte is transferred from the FIFO to either the high- or low-order UNIBUS data register, the microprocessor also receives the data on the M bus and adds it to the partially formed checksum. Thus, the microprocessor is kept busy building the checksum, while the M bus is being used as the data path between the disc interface and the UNIBUS interface. This parallel operation ability of the controller becomes important when the data rate of the disc drive approaches the transfer capacity of the controller because the controller's capacity is directly related to the number of microinstructions that must be executed on each pass through the inner loop of the disc write or disc read code.

THE CLOCK

Figure 9 is a logic diagram of the disc controller clock which is the main source of synchronization signals within the controller. The Am25LS161 provides the ability to select multiples of the basic crystal frequency as the output of the clock circuit (see Table I). The duty cycle of the clock can be varied by adjusting the trimpot on the Am74123 One-Shot.

The crystal is selected to provide the proper frequency for the disc drive to be interfaced. Disc drives based on 2314 technology use the double frequency recording method,

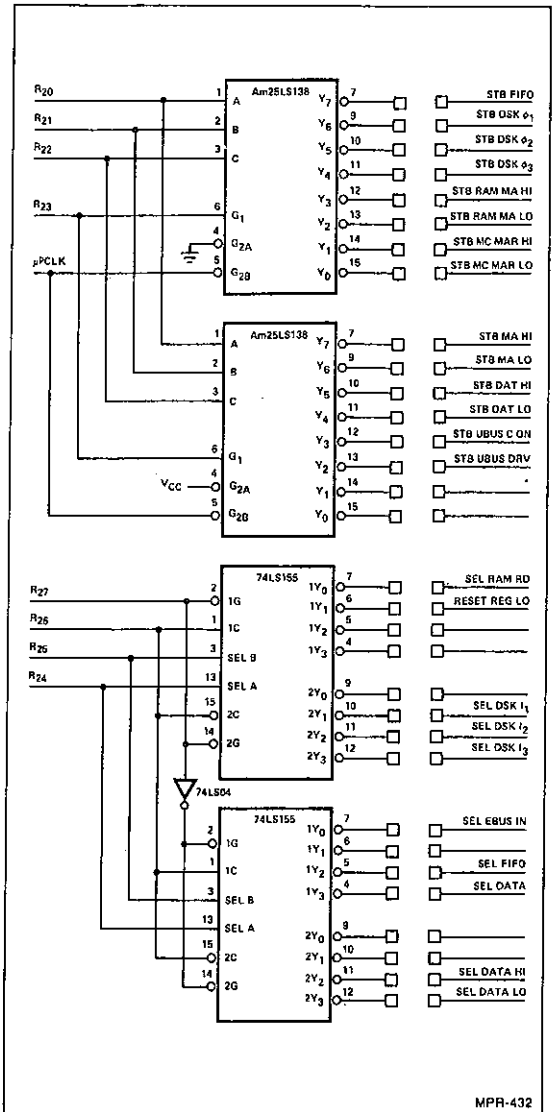


Figure 8.

which means that every other pulse is a clock pulse and the presence or absence of pulses between the clock pulses defines "ones" and "zeros". The crystal frequency must be the same as the double frequency when writing all "ones". If RATE is set to 17, then the frequency of μ PCLK will be one-half the crystal frequency (see Table I), and the microprocessor will cycle once for every data bit received from the disc. This implies that for a 16-bit computer, 16 is the maximum number of microinstructions that can be executed on each pass through the inner loop of the disc read or disc write microcode. (Refer to Appendix I to find examples of the inner loop for reading and writing.) Any more and the controller will gradually fall behind until either the FIFO overflows (disc read) or runs out of data (disc write). It might be possible to clock the microprocessor as fast as it will run, and clock only the FIFO in sync with the disc drive (thus allowing

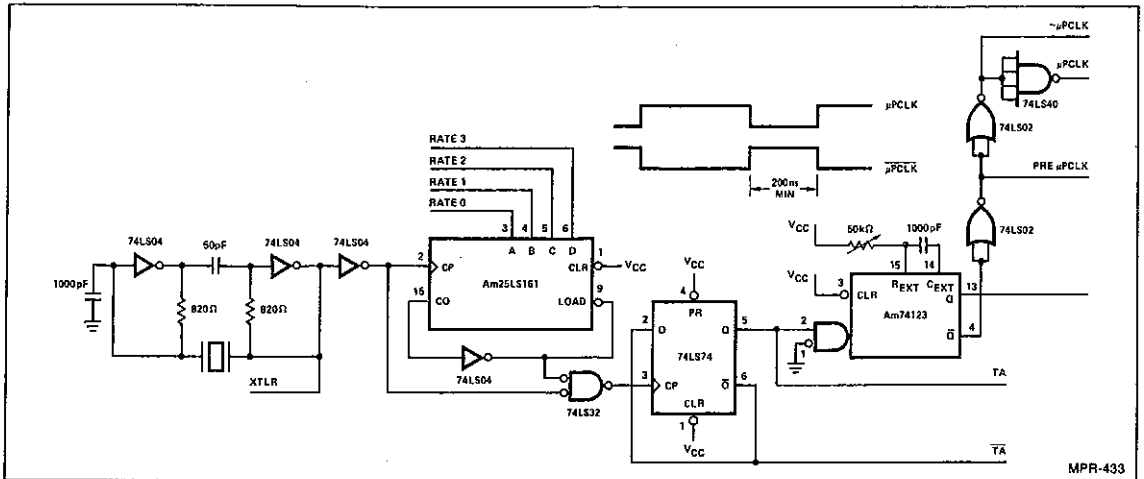


Figure 9.

Rate Input	μPCLK Frequency
17	XTLR/2
16	XTLR/4
15	XTLR/6
14	XTLR/8
13	XTLR/10
12	XTLR/12
11	XTLR/14
10	XTLR/16
7	XTLR/18
6	XTLR/20
5	XTLR/22
4	XTLR/24
3	XTLR/26
2	XTLR/28
1	XTLR/30
0	XTLR/32

Table I. Selecting μPCLK Frequency.

more microinstructions per word transferred), but strange problems with roots based in the beat frequency between the microprocessor clock and the FIFO clock would be likely to occur.

INTERACTION OF CONTROLLER SUB-SECTIONS

Now that each sub-section has been described, it should be instructive to step through a disc transfer operation and observe the interaction of the controller sub-sections. Initially, the controller, in its idle state with no error conditions present, is looping on the SECTOR PULSE condition line. When SECTOR PULSE, a signal from the disc drive, goes "true", the controller loads the address of its control and status register into the UNIBUS address register, sets the control lines for a read operation, and then requests the UNIBUS by asserting NPR REQ. When control has been

granted (signalled by the assertion of NPR RDY), the controller asserts TRAN to start the UNIBUS read cycle. The assertion of TRANSFER DONE signals that the control and status register has been read and the data is in the UNIBUS data register.

If the low-order bit of the control and status register is not set, then no operation has been requested. The controller will fall back into its idle loop as soon as it updates the disc status register, which contains the sector number of the sector currently under the heads.

If the low-order bit was set, then the next low-order three bits define the function to be performed. However, before dispatching to the appropriate routine for whatever function is to be performed, the controller reads the memory address, word count, and disc address for the upcoming transfer from its device registers and copies the data into its internal registers (these are the registers within the Am2901A's). Assuming, for this example, that the function is a disc read, the controller dispatches to the read microcode.

The first microinstruction of the read routine is a subroutine call to the SEEK routine. This routine loads the cylinder address, derived from the disc address, into the output port of the disc interface. The following microinstruction asserts the CYLINDER ADDRESS STROBE on another line in the output port. CYLINDER ADDRESS STROBE is then removed and the controller loops until the drive indicates that the seek has been completed. The SEEK subroutine then selects the proper head (again derived from the disc address) and finally starts looping on SECTOR PULSE. Each time a sector pulse is detected, the controller checks if this is the sector specified in the disc address. If it is, SEEK returns control to the microinstruction following the one that made the call on SEEK. Notice that SEEK doesn't just seek to the desired cylinder, it seeks the sector specified in the disc address.

When control returns to the disc read microcode, the controller waits about 100μs and then asserts READ ENABLE, one of the lines in the output port of the disc interface. At this time, the preamble should be under the enabled head. The preamble is a string of "zeros" terminated by a "one" bit. The "one" bit signals that the data record follows immediately. The first "one" bit will set a flip-flop and assert RD CLK ENABLE (see Figure 2), which will enable the RD CLK from the drive to

start clocking data into the FIFO. Control now falls into the "disc read inner loop" microcode (flowcharted in Appendix I). In this loop, each time a byte is assembled in the FIFO it is copied alternately to the low-order UNIBUS data register and then to the high-order data register. As the data is copied from the FIFO to the data register, the checksum is built by the microprocessor. Every time the high data register is loaded, it is time to transfer another word into PDP-11 main memory. At the end of each UNIBUS transfer, INC MA is asserted to advance the UNIBUS memory address register to the next word address. The transfer word count is then decremented and if not zero another iteration through the "inner loop" is required. When the transfer word count reaches zero, the entire sector has been transferred, and the next word read from the disc is the checksum. This is compared with the checksum that has been built by the microprocessor. If they are not equal, the controller may attempt a retry, or it may just set the checksum error bit in the disc error register and continue as if there were no error. Assuming there wasn't any checksum error, the controller now drops READ ENABLE and the read has been completed. The controller now has only to update its external device registers from the internal set and it is back where first started: in the idle state.

Notice that the external device registers were updated only at the successful completion of the transfer. Therefore, whenever any error condition is encountered, the controller always has the complete information necessary to perform as many retries as the microcode dictates.

SUMMARY

Greater product versatility can be achieved by employing the Am2901A in the design of peripheral controllers. Indeed, there is nothing in the design discussed in this app note that says it has to be a disc controller. The FIFO is the only hardware that "leans" in the direction of a disc controller, and it does so only by virtue of the way it is clocked. But don't forget that the FIFO is just a general purpose, buffered parallel-to-serial and serial-to-parallel converter.

To stress this point of product versatility, let us briefly consider what would be necessary to convert this DEC RK11/RK05 compatible disc controller into a DEC TM11/TU10 mag tape controller. First, remove the FIFO. Next, re-label Figure 6 to read "Mag Tape Interface". Then connect a cable from the mag tape interface to whatever mag tape drive has been selected. Finally, write the microcode that will enable this hardware to emulate the TM11/TM10.

Voilà!

NOTE: Advanced Micro Devices wishes to acknowledge the contributions of William Pitts in the design and implementation of this application note.

¹Microprogramming Handbook; Mick, John R. and Jim Brick, Advanced Micro Devices, 1976.


²PDP-11 Peripherals Handbook, Digital Equipment Corporation, 1975.

PARTS LIST


Device	Description	Qty.	Device	Description	Qty.
Am2901A	Four-Bit Bipolar Microprocessor Slice	2	74S74	Dual D-Flip-Flop, Positive Edge-Triggered	1
Am2907	Quad Bus Transceiver with Three-State Receiver and Parity	5	74LS00	Quad 2-Input NAND Gate	3
Am2911	Microprogram Sequencer	3	74LS02	Quad 2-Input NOR Gate	2
Am29701	Non-Inverting 64-Bit RAM with Three-State Outputs	4	74LS04	Hex Inverter	5
Am29811	Next Address Control Unit	1	74LS08	Quad 2-Input AND Gate	4
Am25LS138	One-of-Eight Decoder/Demultiplexer	2	74LS11	Triple 3-Input AND Gate	1
Am25LS157	Quad 2-Input Multiplexer with Non-Inverting Outputs	1	74LS21	Dual 4-Input AND Gate	1
Am25LS161	Synchronous 4-Bit Binary Counter with Asynchronous Clear	5	74LS32	Quad 2-Input OR Gate	1
Am25LS273	8-Bit Register with Common Clear	12	74LS40	Dual 4-Input NAND Buffer	1
Am25LS374	8-Bit Register with Three-State Outputs	10	74LS55	2-Wide 4-Input AND-OR-Invert Gate	2
Am74123	Dual One-Shot Multivibrator	4	74LS74	Dual D-Flip-Flop, Positive Edge-Triggered	7
Am74LS251	8-Input Multiplexer with Three-State Outputs	2	74LS86	Quad 2-Input Exclusive OR Gate	1
Am74S174	Schottky 6-Bit High Speed Register	2	74LS155	Dual 2-to-4 Decoder/Demultiplexer	3
Am8838	Quad Unified Bus Transceiver	8	8136	6-Bit Unified Bus Comparator, Open Collector	2
Am9130E	1024 x 4 N-Channel Static RAM	12	8837	Single Ended Line Receiver	3
7406	Hex Inverter	5	8881	Quad 2-Input NAND Gate	3
			9403	First-In-First-Out (FIFO) Buffer Memory	2
				TOTAL	120

NOTE: The crystal used in this particular design oscillated at 3.125MHz, and was chosen so that this disc controller would be compatible with the DEC RK11/RK05. Those desiring a different data transmission rate may choose a different crystal to suit their application.

Disk Read Inner Loop

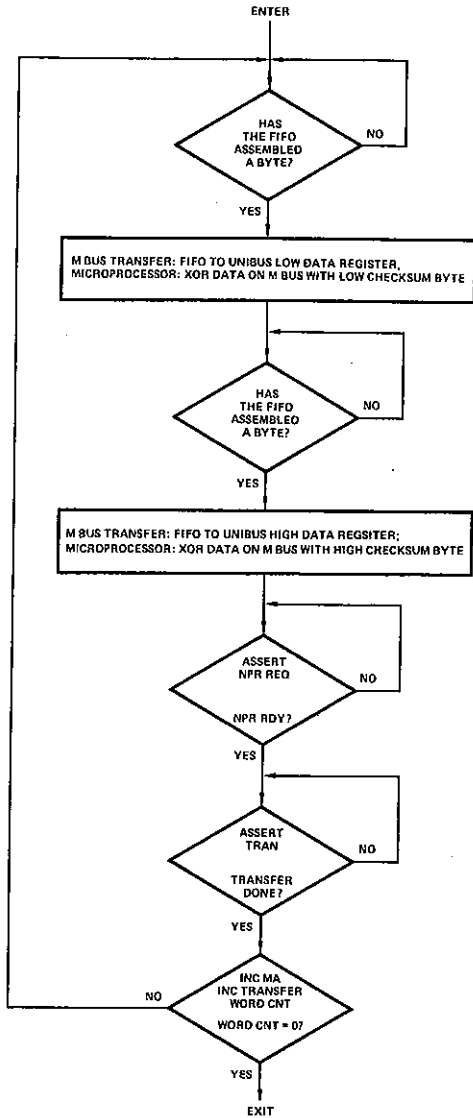

Disk Write Inner Loop

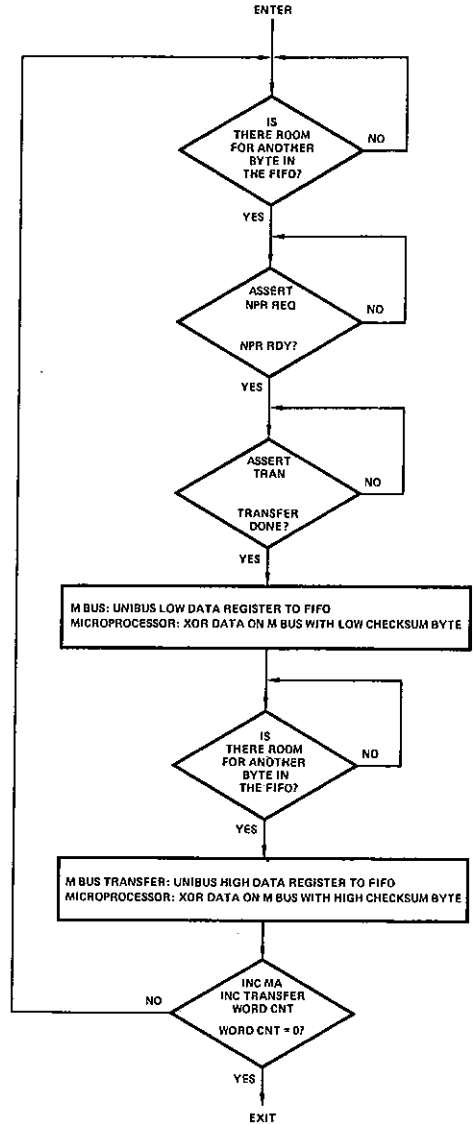

NOTE: Each box represents one microinstruction, but some instructions may be executed more than once.

APPENDIX II

```

/ MICROCODE FOR RK11 SOFTWARE COMPATIBLE DISK CONTROLLER
/ WILLIAM M. PITTS
/ 26 APR 77
    
```

```

/ CONTROL RESET -- RESETS THE DISK CONTROLLER. THIS ROUTINE IS ENTERED
/ WHENEVER 'INIT' IS ASSERTED ON THE UNIBUS OR WHEN
/ THE FUNCTION 'CONTROL RESET' HAS BEEN SPECIFIED BY
/ THE PDP-11.
    
```

```

000 89 A0 60 00 0C 00      /RESET ALL INTERNAL REGS
001 89 A0 70 00 0C 00
002 89 A0 80 00 0C 00
003 89 A0 90 00 0C 00
004 89 A0 A0 00 0C 00
005 89 A0 B0 00 0C 00
006 89 A0 C0 00 0C 00
007 89 A0 DF 60 0C 02      /SET UNIBUS MA TO 177402
008 89 A0 EF 70 0C FF
009 89 A0 FF 01 81 06      /CALL SUB FOR MEM WRITE
    
```

```

/ A DISK OPERATION HAS JUST BEEN COMPLETED, SO SET THE 'DONE' BIT &
/ CLEAR THE 'GO' BIT IN THE INTERNAL RKCS.
    
```

```

00A 75 A8 8F 00 0C 80      /SET 'DONE' BIT IN INTERNAL REG
00B 95 A8 8F 00 0C FE      /CLR 'GO' BIT IN INTERNAL REG
    
```

```

/ NOW IT'S TIME TO UPDATE THE EXTERNAL REGISTERS.
    
```

```

00C 10 A0 3F 00 0C 10      /RESET ERROR RETRY COUNTER
00D 11 AA 6F 60 0C 06      /SET UNIBUS MA TO 177406
00E 11 AB 7F 70 0C FF
00F 00 A0 0F 01 81 06      /CALL SUB TO UPDATE EXT RKWC
010 11 AC 60 00 0C 00
011 11 AD 7F 01 81 07      /UPDATE EXTERNAL RKBA
012 11 AE 60 00 0C 00
013 11 AF 7F 01 81 07      /UPDATE EXTERNAL RKDA
014 11 A8 6F 60 0C 06      /RESET UNIBUS MA TO 177404
015 11 A9 7F 01 81 06      /UPDATE EXTERNAL RKCS
    
```

```

/ IF INTERRUPTS ARE ENABLED, PERFORM INTERRUPT SEQUENCE.
    
```

```

016 94 A8 0F 00 0C 40      /INTERRUPTS ENABLED ?
017 00 A0 0F 00 03 1F      /NO, THEN GO TO 'IDLE'
018 00 A0 0F 40 0C 90      /INTERRUPT VECTOR TO UNIBUS DATA REG
019 00 A0 0F 50 0C 00
01A 00 A0 0F 20 0C 40      /REQUEST UNIBUS FOR INTERRUPT
01B 00 B0 0F 00 03 18      /LOOP HERE TILL WE'VE GOT THE UNIBUS
01C 00 A0 0F 20 0C 60      /ASSERT INTERRUPT
01D 00 00 0F 00 53 10      /LOOP TILL SSYN IS RECEIVED
01E 00 A0 0F 20 0C 00      /RELEASE UNIBUS
    
```

```

/ THE CONTROLLER WAITS FOR SOMETHING TO DO HERE IN THE 'IDLE' LOOP.
/ EVERY TIME A SECTOR PULSE IS SEEN, THE CONTROLLER READS THE EXTERNAL
/ RKCS TO SEE IF A DISK OPERATION HAS BEEN REQUESTED. ALSO, THE EXTERNAL
/ RKDS IS UPDATED AT THIS TIME.
    
```

```

01F 00 A0 0F 60 0C 04      /SET UNIBUS MA TO 177404
020 00 A0 0F 70 0C FF
021 00 B0 0F 00 A3 1F      /LOOP & WAIT FOR SECTOR PULSE
022 00 A0 0F 01 81 00      /READ EXTERNAL RKCS
023 95 A6 8F 08 0C 7F      /MASK & COPY TO INTERNAL REG
024 95 A7 9F 08 0C 0F
025 00 A0 0F 01 81 01      /READ EXTERNAL RKDA
026 11 A6 E0 00 0C 00      /COPY TO INTERNAL RKDA
027 11 A7 FF 60 0C 00
028 00 A0 0F 00 81 82      /SELECT SPECIFIED DISK DRIVE
    
```

```

/ UPDATE EXTERNAL RKDS
    
```

```

029 1D A0 61 00 0C 00      /LOAD SECTOR COUNTER
02A D5 A6 6F 00 0C 40      /SET 'ACCESS READY'
02B 95 A7 7F 00 0C E0      /CLR ALL BUT DRIVE SELECT
    
```

```

02C 05 A7 7F 00 0C 08
02D 00 A0 0F 01 01 06
02E 94 A8 0F 00 0C 01
02F 00 A0 0F 00 03 1F

```

```

JSET 'RK05'
JUPDATE EXTERNAL RKDS
J'GO' BIT SET IN RKCS ?
JNO, THEN LOOP & WAIT

```

```

) A DISK OPERATION HAS BEEN REQUESTED. IF REQUESTED FUNCTION IS
) CONTROL RESET, GO DO IT. ELSE CHECK IF ANY HARD ERRORS ARE PRESENT.
) IF NO HARD ERRORS, UPDATE ALL INTERNAL REGISTERS AND THEN DECODE
) THE REQUESTED FUNCTION AND DISPATCH TO THE APPROPRIATE ROUTINE.

```

```

030 09 A0 1F 01 01 00
031 94 A8 0F 00 0C 0E
032 00 A0 0F 00 03 00
033 95 A6 6F 00 0C FC
034 00 00 0F 01 03 22
035 95 A7 7F 00 0C FF
036 00 00 0F 01 03 22
037 00 A0 0F 60 0C 02
038 00 A0 0F 01 01 06
039 11 A8 60 00 0C 00
03A 11 A9 7F 01 01 07
03B 00 A0 0F 01 01 00
03C 11 A6 A0 00 0C 00
03D 11 A7 0F 01 01 01
03E 11 06 C0 60 0C 00
03F 11 07 00 70 0C 00
040 25 EA C0 00 0C 00
041 25 F8 DF 00 33 43
042 20 A0 00 00 0C 00
043 25 EA C0 00 0C 00
044 25 F8 DF 00 33 46
045 20 A0 00 00 0C 00

```

```

JCLR TEMP ERR REG (NOGO) & READ EXT RKER
JCONTROL RESET ?
JYES, SO DISPATCH
JANY HARD ERRORS ?
JYES, THEN ABORT
JHARD ERRORS ?
JYES, THEN GO TO NOGO
JUPDATE EXT RKER

JCOPY INTERNAL RKCS TO LO & HI
JUPDATE EXT RKCS
JREAD EXT RKWC
J... & COPY TO INTERNAL RKWC
JREAD EXT RKBA
J... & COPY TO INTERNAL RKBA & UNIBUS MA

JUPDATE INT RKBA TO TRANSFER END
.+2

JAGAIN, SINCE RKWC IS A WORD CNT
.+2

```

DISPATCH

```

046 96 A8 0F 00 0C 0E
047 15 A0 0F 00 0C 48
048 10 00 0F 00 02 00
049 00 A0 0F 00 02 50
04A 00 A0 0F 00 02 BC
04B 00 A0 0F 00 02 BC
04C 00 A0 0F 00 02 FC
04D 00 A0 0F 00 02 0C
04E 00 A0 0F 00 02 FE
04F 00 A0 0F 00 02 0A

```

```

JFUNCTION IS LOW 3 BITS OF R0
JUMP TO '. + R0'
JWRITE
JREAD
JWRITE CHECK
JSEEK
JREAD CHECK
JDRIVE RESET
JWRITE LOCK

```

WRITE OPERATION

```

050 95 A8 0F 00 0C 30
051 11 00 00 30 0C 00
052 10 A0 11 00 0C 20
053 95 A1 1F 00 0C 20
054 00 00 0F 01 03 19
055 00 A0 0F 00 01 08
056 00 A0 00 50 0C 00
057 00 A0 0F F0 0C 00
058 00 A0 0F F0 0C 00
059 00 A0 0F E0 0C 03
05A 10 A0 0F 00 0C 2E
05B 00 A0 0F 00 03 5B
05C 00 A0 0F F0 0C 00
05D 20 A0 00 00 0C 00
05E 00 00 0F 00 03 5B

```

```

JMASK OUT ALL BIT MEM EXT BITS
JSET A17, A16, C1, & C0
JREAD SECTOR COUNTER
JDRIVE WRITE LOCKED ?
JYES, SO SET ERR BIT & ABORT
JSEEK TO SPECIFIED CYLINDER
JRESTORE FIFO REGISTERS
JLOAD FIFO WITH 2 '0' BYTES

JASSERT WRITE ENABLE & ERASE ENABLE
JCNTN FOR PREAMBLE BYTES
JLOOP TILL FIFO READY FOR MORE
JFEED FIFO ANOTHER BYTE
JDEC PREAMBLE BYTE CNTN
JITERATE TILL CNTN GOES TO 0

```

```

) THE PREAMBLE IS NOW ON ITS WAY TO THE DISK (SOME OF IT IS STILL IN THE
) FIFO). NEXT WILL BE THE SYNC BIT FOLLOWED BY 2 HEADER BYTES.

```

```

05P 00 A0 0F 00 03 5F
060 00 A0 0F F0 0C 00
061 95 AE 0F 00 0C E0
062 00 A0 0F 00 03 62
063 11 00 00 F0 0C 00
064 95 AF 0F 00 0C 1F

```

```

JWAIT FOR FIFO
JDISPATCH SYNC BIT
JCLR ALL BUT CYLINDER BITS
JWAIT FOR FIFO
JDISPATCH 1ST HEADER BYTE
JREMOVE DRIVE SEL BITS

```

```

065 00 A0 0F 00 D3 65          ;WAIT FOR FIFO
066 11 00 00 F0 0C 00          ;DISPATCH 2ND HEADER BYTE
; THE SYNC BIT & THE 2 BYTE HEADER ARE NOW ON THE WAY TO THE DISK,
; NEXT COMES 512 BYTES OF DATA, BUT 1ST THE DISK WORD COUNT (DWC)
; IS UPDATED BY SUBTRACTING THE UNIBUS WORD COUNT (UWC).

067 29 E1 20 00 0C 00
; WRITE INNER LOOP

068 00 00 0F 04 F3 68          ;INITIATE UNIBUS TRANSFER, WAIT FOR FIFO & UBUS
069 15 A4 48 F0 0C 00          ;COPY DATA TO FIFO & BUILD CHECKSUM
06A 00 00 0F 08 33 6C          ;BUMP MA, CARRY INTO HI CHECKSUM BYTE ?
06B 00 E0 50 00 0C 00          ;YES, SO INC CHK1
06C 00 A0 0F 00 03 0D          ;WAIT FOR FIFO
06D 15 A5 5A F0 0C 00          ;COPY DATA & BUILD CHECKSUM
06E 00 E0 10 00 0C 00          ;UNIBUS WC EXHAUSTED ?
06F 00 00 0F 00 03 68          ;NO, THEN WRITE ANOTHER WORD TO DISK
070 10 A2 00 00 0C 00          ;DISK WC ALSO EXHAUSTED ?
071 00 00 0F 00 03 07          ;NO, THEN WRITE '0'S TILL IT IS

; 512 DATA BYTES ARE ON THE WAY TO THE DISK. NEXT COMES 2 CHECKSUM BYTES
; AND THEN THE POSTAMBLE.

072 00 A0 0F 00 03 72          ;WAIT FOR FIFO
073 11 04 40 F0 0C 00          ;DISPATCH LO CHK BYTE
074 00 A0 0F 00 D3 74          ; ... & NOW HI CHK BYTE
075 11 05 50 F0 0C 00

; POSTAMBLE

076 10 A0 0F 00 0C 06          ;WAIT FOR FIFO
077 00 A0 0F 00 D3 77          ;DISPATCH A PIECE OF THE POSTAMBLE
078 00 A0 0F F0 0C 00          ;MORE POSTAMBLE TO COME ?
079 2D A0 00 00 0C 00          ;YES, SO ITERATE
07A 00 A0 0F 00 03 00

; POSTAMBLE IS ON ITS WAY TO THE DISK. NOW WE MUST WAIT FOR FIFO TO
; EMPTY BEFORE THE WRITE CURRENTS ARE DISABLED.

07B 00 00 0F 00 C3 7A          ;FIFO OUTPUT REG EMPTY ?
07C 00 00 0F 00 C3 7B          ;MAKE SURE WE DIDN'T SEE BETWEEN BYTE GLITCH

; 'NXTSEC' WILL DISABLE THE WRITE OR READ CURRENTS AND CHECK IF MORE
; DATA IS TO BE READ OR WRITTEN BEYOND THE SECTOR THAT HAS JUST BEEN
; COMPLETED. IF MORE IS CALLED FOR, 'DOSEEK' WILL BE CALLED TO
; POSITION THE HEADS FOR THE NEXT SECTOR & THEN CONTROL WILL BE RETURNED
; TO THE READ OR WRITE ROUTINE.

07D 00 E0 EF E0 0C 00          ;BUMP DA TO NEXT SECTOR, DISABLE CURRENTS
07E 95 AE 0F 00 0C 0F          ;COPY JUST SECTOR TO R0
07F 34 E0 0F 00 0C 0C          ;OVERFLOW TO NEXT TRACK ?
080 00 00 0F 00 03 84          ;NO, THEN GO TO 'MORE'
081 15 AE EF 00 0C 04          ;NEXT TRACK, SECTOR 0
082 00 00 0F 00 33 84          ;CARRY OUT OF RKDA0 ?
083 00 E0 F0 00 0C 00          ;YES, SO BUMP RKDA1
084 10 AB 00 00 0C 00          ;ANY MORE TO TRANSFER ?
085 00 A0 0F 00 03 0A          ;NO, THEN WE'RE ALL DONE
086 94 AE 0F 00 0C 1F          ;NEED SEEK TO NEW CYLINDER ?
087 00 00 0F 00 03 A4          ;NO, PRETEND SEEK JUST COMPLETED

; 'DOSEEK' IS THE ROUTINE THAT SEEKS TO THE CYLINDER ADDRESSED IN THE
; INTERNAL RKDA. AFTER THE SEEK HAS BEEN COMPLETED, 'OKSEEK' WILL
; WAIT UNTIL THE SPECIFIED SECTOR IS JUST BEFORE THE HEADS (SECTOR PULSE
; IS SEEN) AND THEN RETURN TO THE CALLING ROUTINE.

088 95 AE 0F 00 0C 0F          ;COPY SECTOR BITS TO R0
089 34 E0 0F 00 0C 0C          ;LEGAL SECTOR NUMBER ?
08A 00 00 0F 01 13 10          ;NO, THEN TAKE ERROR EXIT
08B 95 AE 6F 00 0C E0          ;COPY CYL BITS TO LO, HI
08C 95 AF 7F 00 0C 1F          ;LOAD LOW CYL REG
08D 10 86 00 00 0C 00

```

08E 10 87 00 C0 0C 00
08F 00 A0 0F E0 0C 00

! ... & HIGH CYL REG
! INITIATE SEEK

! THE SEEK HAS JUST BEEN INITIATED, NOW LOOP ON CHECKING FOR SEEK ERROR
! OR SEEK DONE.

090 10 A0 02 00 0C 00
091 00 A0 0F E0 0C 00
092 00 B0 0F 01 03 14
093 10 A0 01 00 0C 00
094 05 A0 0F 00 0C 40
095 00 B0 0F 00 03 90

!GET ERROR BITS
!DROP 'STBCYL'
!IF ERR, GO TO 'UNSAFE'
!READ SECTOR COUNTER
!BUSY SEEKING ?
!YES, SO LOOP

! SEEK COMPLETE, NOW READ HEADER OF NEXT SECTOR THAT COMES BY AND
! VERIFY THAT THIS IS THE CORRECT CYLINDER, UNLESS THIS IS A
! FORMAT READ IN WHICH CASE THERE IS NO CYLINDER VERIFICATION.

096 94 A9 0F 00 0C 04
097 00 B0 0F 00 03 A4
098 00 B0 0F 00 A3 98
099 10 A0 0F 00 0C 80
09A 2D A0 00 00 0C 00
09B 00 B0 0F 00 03 9A
09C 00 A0 00 50 0C 00
09D 00 A0 0F E0 0C 04
09E 00 A0 0F 00 C3 9E
09F 34 E6 0E 00 0C 00
0A0 00 B0 0F 01 03 18
0A1 00 A0 0F 00 C3 A1
0A2 34 E7 0E 00 0C 00
0A3 00 B0 0F 01 03 18

!FORMAT READ ?
!YES, SO BYPASS VERIFICATION
!WAIT FOR SECTOR PULSE
!LOAD DELAY COUNTER
!WAIT FOR PREAMBLE TO GET UNDER HEADS
!WAIT LOOP
!RESTORE FIFO REGISTERS
!ASSERT READ ENABLE
!WAIT FOR 1ST HEADER BYTE
!LOW CYL ADDR OK ?
!NO, THEN SEEK ERROR
!WAIT FOR 2ND HEADER BYTE
!HIGH CYL ADDR OK ?
!NO, THEN SEEK ERROR

! GOOD SEEK, NOW INITIALIZE CHECKSUM REGISTERS TO ZERO, SET UNIBUS
! WORD COUNT TO WHATEVER IT SHOULD BE, & SET DISK WORD COUNT FOR ONE
! SECTOR (256 WORDS).

0A4 89 A0 40 00 0C 00
0A5 89 A0 50 00 0C 00
0A6 89 A0 20 00 0C 00
0A7 89 A0 10 00 0C 00
0A8 00 E0 00 00 0C 00
0A9 00 B0 0F 00 03 AD
0AA 11 AA 10 00 0C 00
0AB 89 A0 A0 00 0C 00

!CLR CHECKSUM REGISTERS
!256, WORD DISK TRANSFER
!ASSUME ALL OF SECTOR WANTED
!FULL SECTOR TRANSFER ?
!'OKSEEK' IF MORE THAN FULL SECTOR
!SET UNIBUS WORD COUNT
!CLK INTERNAL RWKC (LAST SECTOR)

! SELECT HEAD

0AC 00 A0 0F 00 01 02

! AT 'OKSEEK', EVERYTHING IS SET UP FOR THE UPCOMING TRANSFER, NOW
! THE CONTROLLER WILL WAIT UNTIL THE SPECIFIED SECTOR IS JUST REACHING
! THE HEADS BEFORE RETURNING TO THE CALLER,

0AD 00 B0 0F 00 A3 AD
0AE 04 AE 01 00 0C 00
0AF 94 A0 0F 00 0C 0F
0B0 00 B0 0F 00 03 AD
0B1 00 A0 0F 00 8A 00

!WAIT FOR SECTOR PULSE
!SPECIFIED SECTOR ?
!DON'T KNOW TILL WE CLEAN IT UP
!NOT SECTOR WE WANT
!RETURN

! 'SELECT' SELECTS THE HEAD SPECIFIED IN THE INTERNAL RK0A.

0B2 05 AE 6F 00 0C 10
0B3 10 86 00 00 0C 00
0B4 00 A0 0F 00 8A 00

!COPY HEAD SEL BIT TO 'LD'
!SELECT HEAD
!RETURN

! 'WRITEZ' APPENDS ZEROS TO SHORT RECORDS AS THEY ARE WRITTEN ON
! THE DISK.

0B5 00 E0 20 00 0C 00
0B6 00 A0 0F 00 03 72
0B7 00 A0 0F 00 03 87
0B8 00 A0 0F F0 0C 00
0B9 00 A0 0F 00 03 89

!MARK PASSAGE OF ANOTHER WORD TO DISK
!'WRTOON' WHEN DONE
!WAIT FOR FIFO
!DISPATCH A ZERO
!WAIT

0BA 00 A0 0F F0 0C 00
0BB 00 A0 0F 00 02 85

JPAD
JLOOP

); READ OPERATIONS == READ, READ CHECK, & WRITE CHECK ALL TRANSFER HERE.

0BC 94 80 0F 30 0C 32
0BD 00 A0 0F 00 81 88
0BE 10 A0 0F 00 0C 80
0BF 20 A0 00 00 0C 00
0C0 00 80 0F 00 03 8F
0C1 00 A0 00 50 0C 00
0C2 00 A0 0F E0 0C 04
0C3 00 A0 0F 00 C3 C3
0C4 10 A0 6E 00 0C 00
0C5 00 A0 0F 00 C3 C5
0C6 10 A0 7E 00 0C 00
0C7 94 A9 0F 00 0C 04
0C8 00 80 0F 00 03 F6
0C9 94 A8 0F 00 0C 02
0CA 00 80 0F 00 03 0F
0CB 25 E1 20 00 0C 00

JSET A17, A16, C1, & C0
JSEEK
JLOAD DELAY COUNTER
JWAIT FOR PREAMBLE TO GET UNDER HEADS
JWAIT LOOP
JRESTORE FIFO REGISTERS
JASSERT READ ENABLE
JWAIT FOR 1ST HEADER BYTE
JGET 1ST HEADER BYTE
JWAIT FOR 2ND HEADER BYTE
J... & STICK IT IN 'HI'
JFORMAT READ ?
JYES, SO TRANSFER JUST HEADER BYTES
JREAD OR WRITE CHECK ?
JYES
JUPDATE DISK WORD COUNT

); DISK READ INNER LOOP

0CC 00 A0 0F 00 C3 CC
0CD 15 A4 4E 40 0C 00
0CE 00 80 0F 08 33 D0
0CF 0D E0 50 00 0C 00
0D0 00 80 0F 00 E3 D0
0D1 15 A5 5E 50 0C 00
0D2 00 E0 10 04 0C 00
0D3 00 80 0F 00 03 CC
0D4 10 A2 00 00 0C 00
0D5 00 80 0F 00 03 E1

JWAIT FOR DATA
JCOPY DATA & BUILD CHECKSUM
JBUMP MA, CARRY INTO CHK1 ?
JYES, SO SEE THAT IT GETS THERE
JWAIT FOR DATA & UNIBUS
JCOPY & BUILD
JSTART UNIBUS TRANSFER, THIS LAST WORD ?
JNO, THEN GO READ NEXT WORD
JMORE DATA STILL IN SECTOR ?
JYES, SO CONT TO BUILD CHECKSUM

); DATA HAS JUST BEEN READ. NOW READ & VERIFY CHECKSUM.

0D6 00 A0 0F 00 C3 06
0D7 35 E4 4E 00 0C 00
0D8 00 80 0F 00 33 DA
0D9 20 A0 50 00 0C 00
0DA 00 A0 0F 00 C3 DA
0DB 35 E5 5E 00 0C 00
0DC 64 A4 5F E0 0C 00
0DD 00 80 0F 01 03 0E
0DE 00 A0 0F 00 02 7D

JWAIT FOR 1ST CHECKSUM BYTE
JSUB LOW CHECKSUM BYTES
JDON'T FORGET THE CARRY
JOK
JOK
JWAIT FOR 2ND CHECKSUM BYTE
JSUB HIGH CHECKSUM BYTES
JCHECKSUM ERROR ? DISABLE READ CURRENT
JNO, THEN ERROR
JIF MORE, CONT TO NEXT SECTOR

); READ & WRITE CHECK TRANSFER TO 'RDCK0'. NOW TEST TO SEE WHICH IT IS AND BRANCH ACCORDINGLY.

0DF 94 A8 0F 00 0C 04
0E0 00 80 0F 00 03 EA

JREAD CHECK ?
JNO, SO MUST BE WRITE CHECK

); READ CHECK INNER LOOP

0E1 00 A0 0F 00 C3 E1
0E2 15 A4 4E 00 0C 00
0E3 00 80 0F 00 33 E5
0E4 0D E0 50 00 0C 00
0E5 00 A0 0F 00 C3 E5
0E6 15 A5 5E 00 0C 00
0E7 0D E0 20 00 0C 00
0E8 00 80 0F 00 03 E1
0E9 00 A0 0F 00 02 06

JWAIT FOR DATA
JBUILD CHECKSUM
JCAHRY ?
JYES
JWAIT FOR DATA
JBUILD CHECKSUM
JBUMP DISK WORD COUNT
JLOOP THRU ALL OF SECTOR
J... & THEN GO TO 'RDONE'

); WRITE CHECK INNER LOOP

0EA 00 A0 00 04 0C 00
0EB 00 A0 0F 00 03 00
0EC 10 A0 6E 00 0C 00
0ED 34 E6 00 00 0C 00
0EE 00 80 0F 01 03 0C
0EF 10 A0 6A 00 0C 00

JSTART UNIBUS READ
JWAIT FOR DATUM FROM BOTH SOURCES
JGET DISK DATA BYTE
JSUB BYTE FROM MEMORY
JERROR IF NOT 0
JGET BYTE FROM MEMORY

```

0F0 00 A0 0F 00 C3 F0          ;WAIT FOR DISK DATA
0F1 34 E6 0E 00 0C 00          ;SUB BYTE FROM DISK
0F2 00 80 0F 01 03 0C          ;ERROR IF NOT 0
0F3 00 E0 10 00 0C 00          ;JUMP UNIBUS WORD CNT
0F4 00 80 0F 00 03 EA          ;LOOP TILL DONE
0F5 00 A0 0F 00 02 FA          ;JOIN FORMAT READ STREAM

```

```

; FORMAT READ -- THE 2 HEADER BYTES ARE IN 'LO' & 'HI'. TRANSFER THEM
; TO MAIN MEMORY & ITERATE TILL UNIBUS WORD COUNT IS 0.

```

```

0F6 11 E1 A0 00 0C 00          ;INTERNAL RKWC NEEDS UPDATE
0F7 00 A0 0F 00 03 F9          ;UNDO WHAT 'SEEK' DID
0F8 20 A0 B0 00 0C 00          ;TRANSFER HEADER
0F9 00 A0 0F 01 81 07          ;IF MORE, CONT TO NEXT SECTOR
0FA 00 A0 0F 00 81 7D          ;REENTER READ STREAM
0FB 00 A0 0F 00 02 BE

```

```

; SEEK ROUTINE -- SINCE SEVERAL RKWS DRIVES ARE MAPPED ONTO THE PERTEC
; DRIVE, IT IS BEST TO SEEK ONLY BEFORE PERFORMING A DATA TRANSFER.

```

```

0FC 75 A9 9F 00 0C 20          ;SET 'SEARCH COMPLETE' IN RKCS
0FD 00 A0 0F 00 02 0A          ;WE'RE DONE !

```

```

; DRIVE RESET -- RECALIBRATE & BRANCH TO 'SEEK'

```

```

0FE 00 A0 0F 01 81 2B          ;RECALIBRATE
0FF 00 A0 0F 00 02 FC          ;JOIN UP WITH 'SEEK'

```

```

; UNIBUS DATA TRANSFER SUBROUTINES

```

```

100 00 A0 0F 30 0C 30          ;INITIAL DATA IN ENTRY POINT
101 00 A0 00 04 0C 00          ;INITIATE TRANSFER
102 00 B0 0F 01 63 02          ;WAIT FOR UNIBUS
103 1D A0 6B 00 0C 00          ;GET LOW DATA BYTE
104 1D A0 7A 00 0C 00          ;... & HIGH DATA BYTE
105 00 A0 0F 08 8A 00          ;RETURN

```

```

106 00 A0 0F 30 0C 32          ;INITIAL DATA OUT ENTRY POINT
107 1D 86 00 40 0C 00          ;COPY LOW DATA
108 1D 87 00 50 0C 00          ;... & HIGH DATA
109 00 A0 00 04 0C 00          ;INITIATE TRANSFER
10A 00 B0 0F 01 63 0A          ;WAIT FOR 'TRANSFER DONE'
10B 00 A0 0F 08 8A 00          ;RETURN

```

```

; ERROR ROUTINES -- ALL ERRORS ARE HANDLED IN THE SAME MANNER.
; 1ST THE APPROPRIATE ERROR BIT IS SET IN THE INTERNAL ERROR REGISTER
; (R0, UNC), AND THEN THE INTERNAL RKCS IS CHECKED TO SEE IF
; 'STOP ON SOFT ERROR' IS SET. IF NOT, THEN 'RETRY' WILL BE CALLED
; TO ATTEMPT THE COMPLETE TRANSFER ONCE AGAIN. UP TO 16 RETRIES WILL
; BE ATTEMPTED AUTOMATICALLY. IF THE ERROR CONDITION PERSISTS, OR
; 'STOP ON SOFT ERROR' IS SET, THE EXTERNAL RKER WILL BE READ AND ORED
; WITH THE INTERNAL ERROR REGISTER & THEN THE EXTERNAL RKER WILL BE
; UPDATED WITH THIS NEW ERROR DATA. FINALLY, THE EXTERNAL RKCS WILL
; BE UPDATED WITH THE APPROPRIATE ERROR BITS & CONTROL WILL TRANSFER
; TO 'DONE'.

```

```

10C 1D A0 0F 00 0C 01          ;SET 'WCE' IN RKER0
10D 00 A0 0F 01 02 13

```

```

10E 1D A0 0F 00 0C 02          ;SET 'CSE' IN RKER0
10F 00 A0 0F 01 02 13

```

```

110 1D A0 0F 00 0C 20          ;SET 'NYS' IN RKER0
111 00 A0 0F 01 02 13

```

```

112 1D A0 0F 00 0C 40          ;SET 'NXC' IN RKER0
113 89 A0 1F 01 02 1A          ;CLR RKER1, GO TO 'ERROR'

```

```

114 94 A0 0F 00 0C 02          ;SEEK INCOMPLETE ?
115 00 B0 0F 01 03 12          ;YES, THEN PRETEND 'NXC'
116 1D A0 1F 00 0C 80          ;SET 'DRE' IN RKER1
117 00 A0 0F 01 02 19

```



```

118 1D A0 1F 00 0C 10
119 89 A0 00 00 0C 00
11A 94 A9 0F 00 0C 01
11B 00 B0 0F 01 03 1E
11C 2D A0 30 00 0C 00
11D 00 B0 0F 01 03 29
11E 00 A0 0F 60 0C 02
11F 00 A0 0F 70 0C FF
120 00 A0 0F 01 81 00
121 65 A0 60 00 0C 00
122 65 A1 7F 60 0C 02
123 00 A0 0F 01 81 06
124 75 A9 9F 00 0C 80
125 94 A0 0F 00 0C 03
126 00 B0 0F 00 03 0A
127 75 A9 9F 00 0C 40
128 00 A0 0F 00 02 0A

129 00 A0 0F 01 81 20
12A 00 A0 0F 00 02 1F

12B 00 A0 0F C0 0C 40
12C 00 A0 0F E0 0C 00
12D 00 A0 00 00 0C 00
12E 00 A0 0F E0 0C 00
12F 1D A0 01 00 0C 00
130 94 A0 0F 00 0C 40
131 00 A0 0F 01 03 2F
132 00 A0 0F 00 0A 00

```

```

ISET 'SKE' IN RKER1
ICLR RKER0
ISTOP ON SOFT ERROR ?
IYES
IDEC ERR CNTR, TIME TO GIVE UP ?
INO, SO TRY AGAIN
ISET MA = 177402 (RKER)

```

```

IREAD EXTERNAL RKER
IUPDATE OLD RKER
IPRESET MA TO 177402
IWRITE UPDATED RKER
ISET 'ERRDR' IN RKC81
ISOFT ERROR ?
IYES
INO, SO SET 'HE' IN RKC81
IRETURN IN DISGRACE

```

```

IRECALIBRATE
/ ... & TRY AGAIN

```

```

IASSERT 'RESTORE'
IASSERT 'STBCYL'
/PAUSE
IREMOVE 'STBCYL'
ILOOP TILL NOT 'BUSY'
IBUSY ?
IYES
IEXIT

```

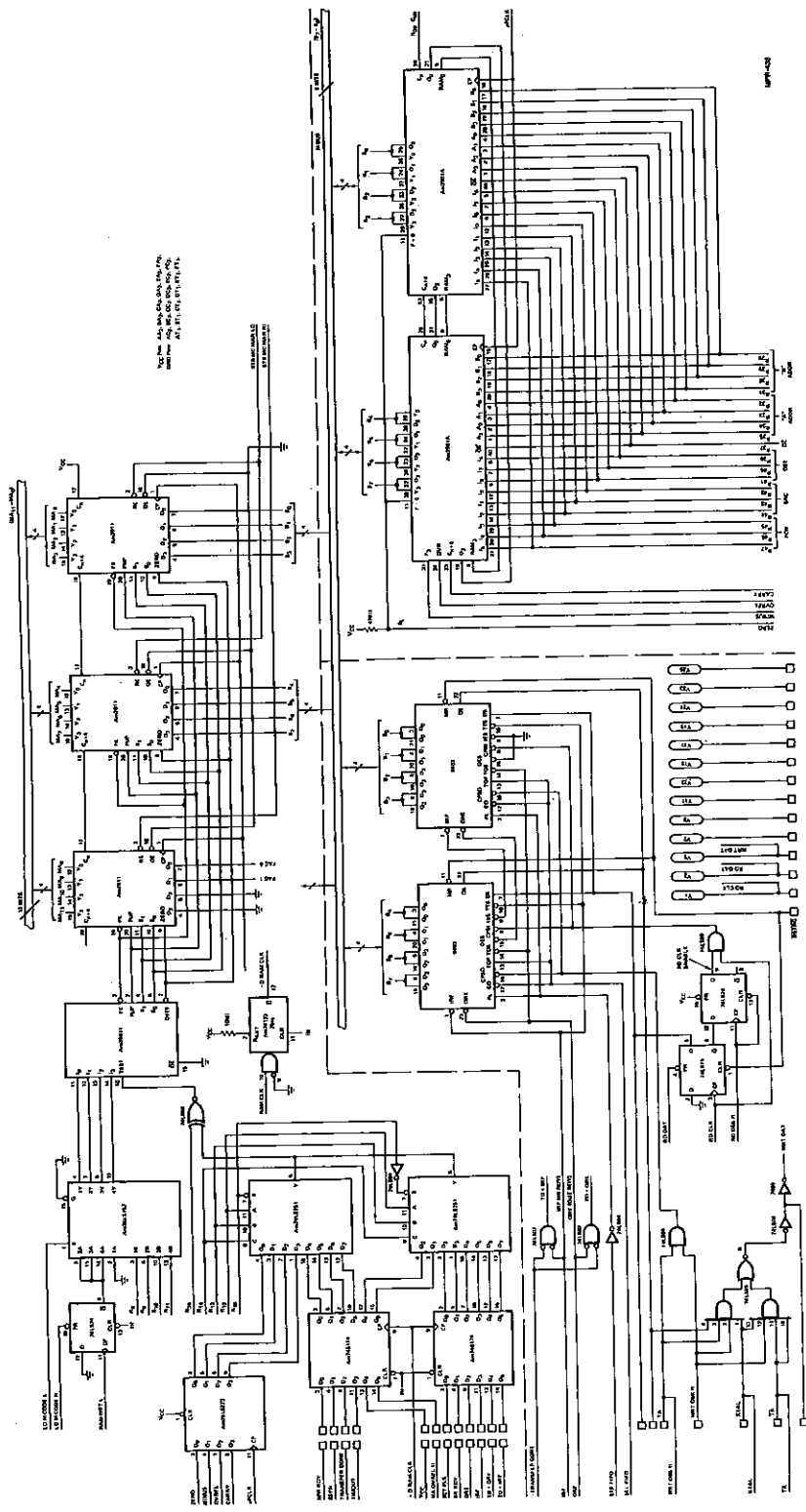


Figure 2.

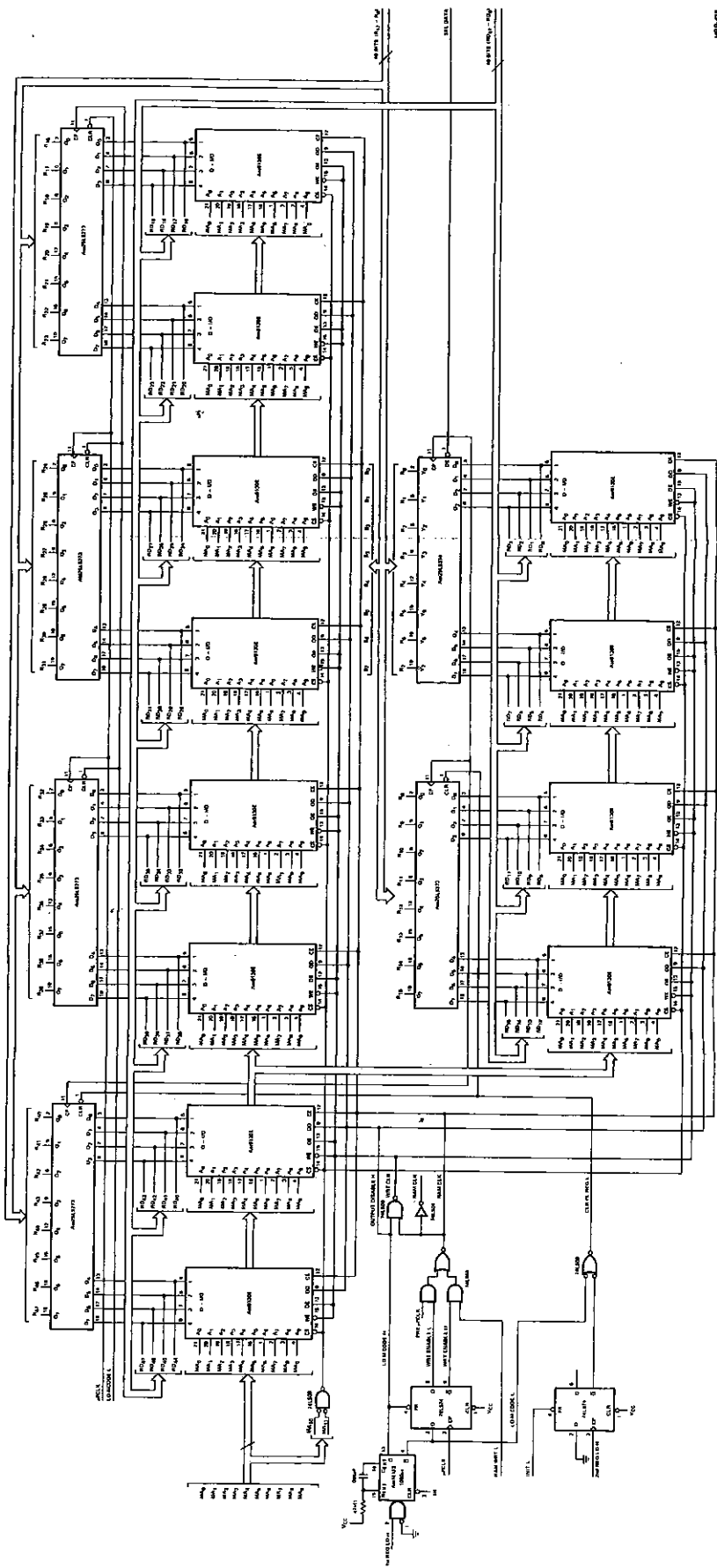


Figure 4.

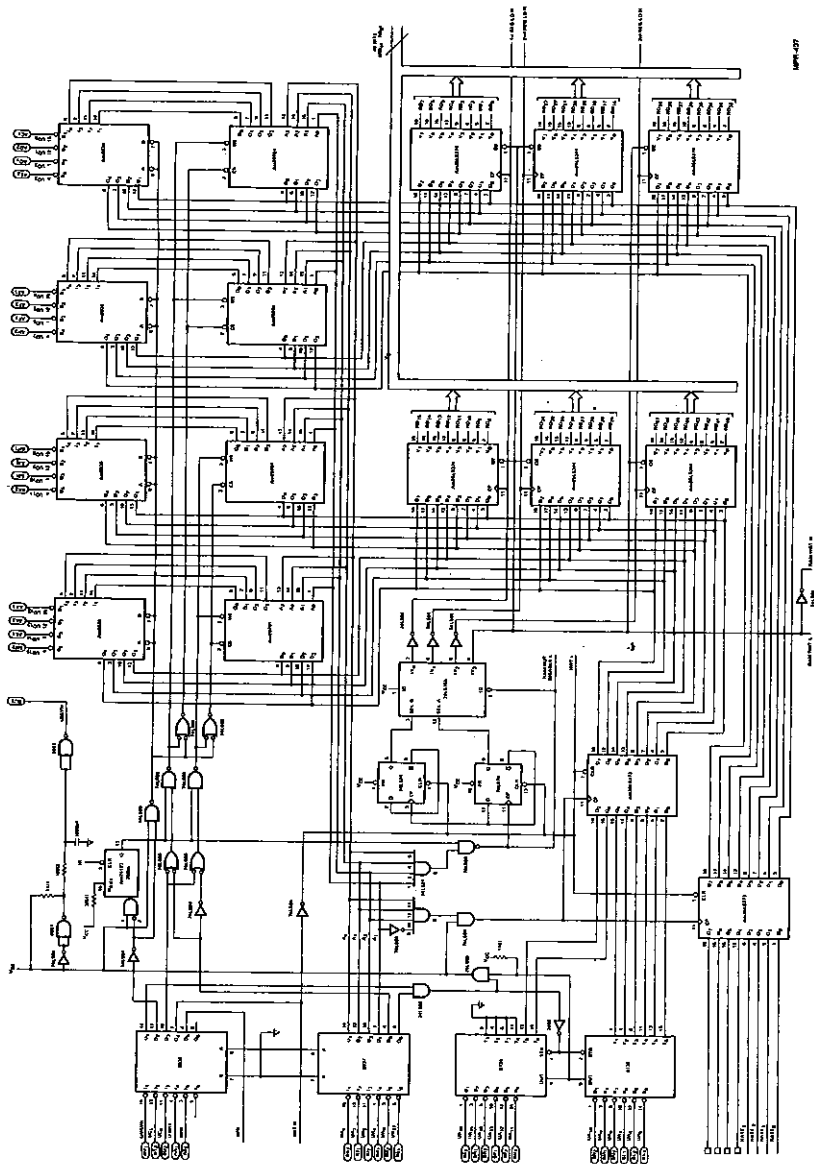


Figure 6.

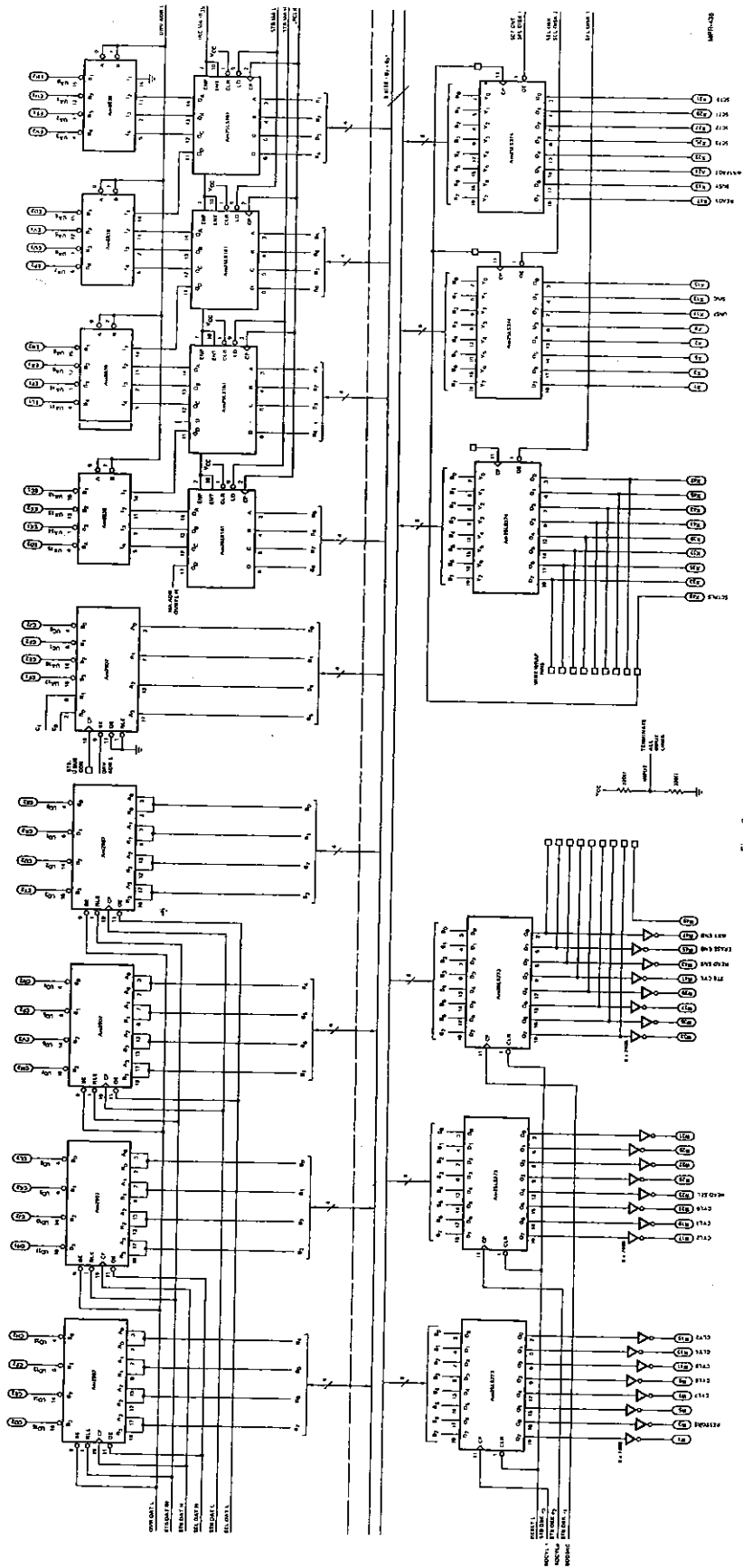


Figure 6.